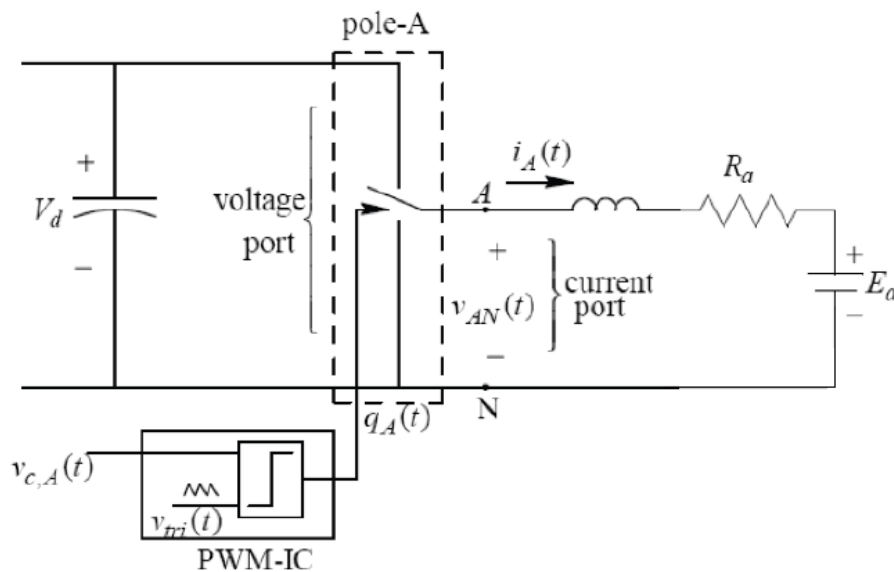


Switched converter pole



$$\Rightarrow i'(t) = v_{AN}(t)/L - E/L - (R/L) \cdot i(t) \quad (II)$$

v_{AN} is controlled by the switched converter. When $V_{cA} \geq v_{tri}$, $v_{AN} = V_d$; and $v_{AN} = 0$ otherwise.

Here's how we can model this in Acumen. Let's start by creating our v_{tri} signal as a saw-tooth wave between zero and 10, and frequency 1KHz.

```
class TriggerSource()
    private Vtri=0; Vtri'=1000; end
    Vtri' [=] 1000;
    if Vtri >= 10 Vtri=0; end
end
```

We need v_{tri} to go from 0 to 10 in 0.001 seconds, so we set its derivative to $10/0.001=10000$. When v_{tri} reaches 10, we reset it to zero. Next we model the switched converter. This class depends on two variables, the source voltage V_d and the control voltage V_{cA} .

```
class SwitchedConverter(Vd,Vca)
    private Van = 0; trigger = create TriggerSource(); end
    if trigger.Vtri >= Vca Van [=] Vd; else Van [=] 0; end
end
```

The equivalent circuit in this case can be modeled with equation (II). Don't forget to instantiate the switched converter with $V_d=100$ and $V_{cA}=8$.

```
class EquivalentCircuit(R,L,E)
    private i=0; i'=0;
    converter = create SwitchedConverter(100,8);
end
```

```
    i' [=] converter.Van/L - E/L - (R/L)*i;  
end
```

We finish our model by instantiating our equivalent circuit in [Main](#).

```
class Main(simulator)  
    private circuit = create EquivalentCircuit(0.5,0.012,40);  
end  
    simulator.timeStep = 0.0001;  
    simulator.endTime = 0.1;  
end
```